



Welcome to The Logic Design Lab!

Fall 2021
Midterm Review

Prof. Chun-Yi Lee

Department of Computer Science
National Tsing Hua University

Announcements

- Lab 3
 - Basic questions demonstration on **10/21/2021 (Thu)**
 - Advanced questions and FPGA demonstration due on **10/28/2021 (Thu)**
- Lab 4
 - Lab 4 basic questions demonstration on **11/2/2021 (Tue)**
- Midterm Exam
 - Computer-based exam on **11/4/2021 (Thu)**
- Final Project Proposal (5%)
 - Please submit your proposal (1~2 pages) by **12/13/2021 (Mon)**
 - Briefly describe your project contents
 - Be creative!

Agenda

- Gate-Level Design and Basic Concepts
- Data Flow Modeling
- Behavioral Modeling
- Sequential Circuits
- Debounce and One-Pulse Circuits
- FPGA Implementation

Today's class will help you:

1. Review the contents of this course

Primitive Logic Gates

- Basic Logic gates are provided as pre-defined primitives
 - **and, or, xor, nand, nor, xnor, not**
- The first terminal is the output and the rests are the inputs
 - How to use them? Easy!

wire	OUT, IN, IN1, IN2;
and	a1(OUT, IN1, IN2);
nand	na1(OUT, IN1, IN2);
or	or1(OUT, IN1, IN2);
nor	nor1(OUT, IN1, IN2);
xor	x1(OUT, IN1, IN2);
xnor	nx1(OUT, IN1, IN2);
not	n1(OUT, IN);

Smart Primitives

```
module      nand3 (O, A1, A2, A3);
```

```
    input      A1, A2, A3;
```

```
    output     O;
```

```
nand      NAND1 (O, A1, A2, A3);
```


```
endmodule
```

Remember to give a name for it!

- Same primitive can be used to describe for **arbitrary number** of inputs
- Except for “**not**”, which takes **ONLY ONE** input
- Not gate can generate **multiple number of outputs**
 - E.g., not U (O1, O2, ..., ON, IN), where O1~ON equal the inverse of IN


Array of Instances
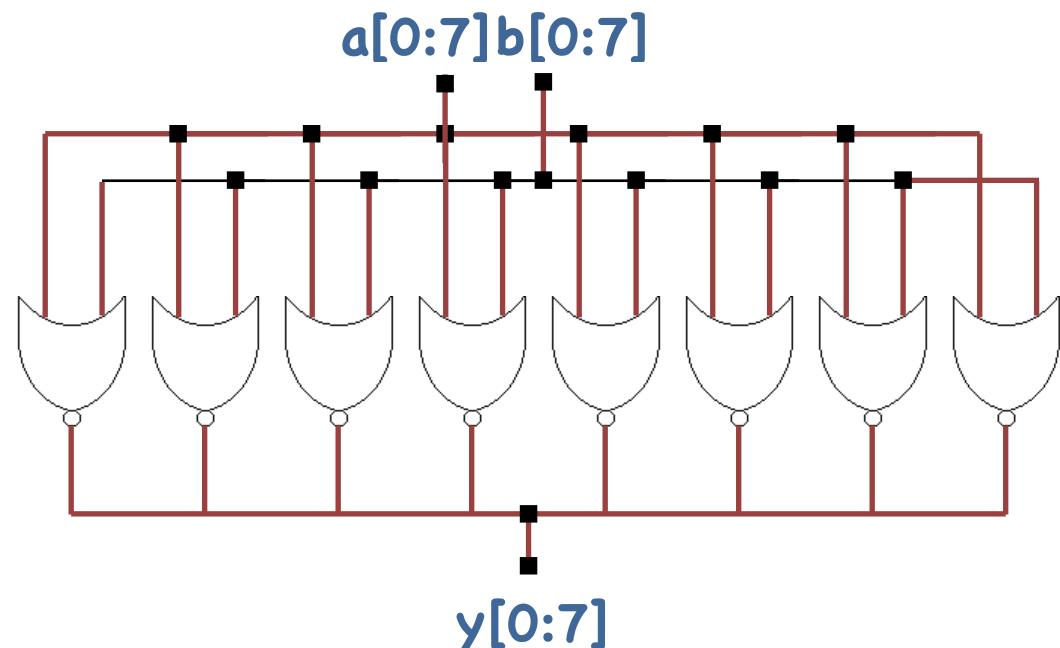
```
module array_of_nor (y, a, b);  
    input [7:0] a, b;  
    output [7:0] y;  
  
    nor Nor_Array [7:0] (y, a, b);  
  
endmodule
```



Hierarchy of Modules (1/2)

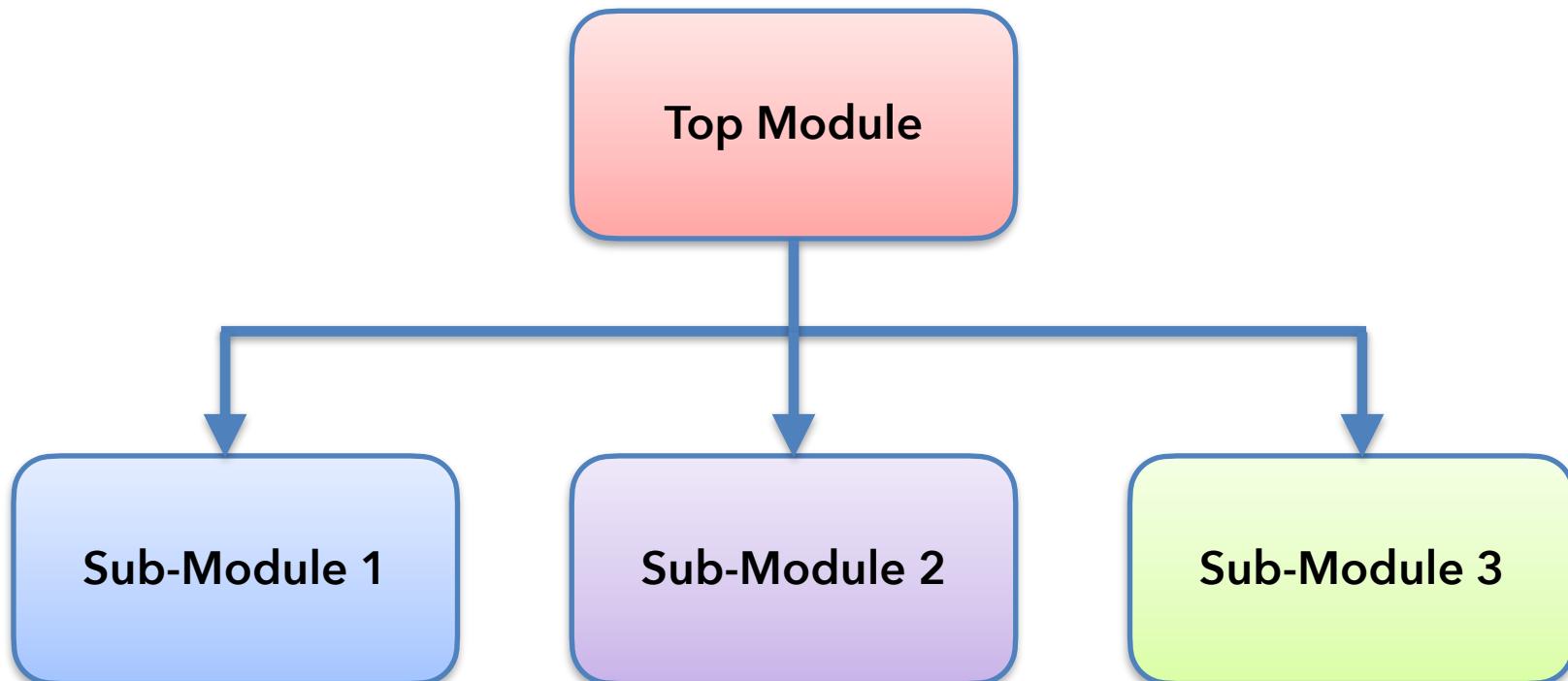- A typical Verilog design consists of multiple hierarchies of modules
- A module may be implemented by several sub-modules
- The outermost module is called the “**top module**”



Port Mapping

- Port mapping can be done in either of the following two ways

Connect by ordered lists

```
module red (x1, x2, y1, y2);  
    input x1, x2;  
    output y1, y2;  
    wire w1, w2, w3;  
    green U1 (x1, x2, w1, w2, w3);  
    blue U2 (w1, w2, w3, y1, y2);  
endmodule
```


Connect by port names

```
module red (x1, x2, y1, y2);  
    input x1, x2;  
    output y1, y2;  
    wire w1, w2, w3;  
    green U1 (.b(x2), .c(w1), .a(x1), .d(w2), .e(w3));  
    blue U2 (.i(y1), .j(y2), .f(w1), .g(w2), .h(w3));  
endmodule
```

Port order can be random!

Fan-outs

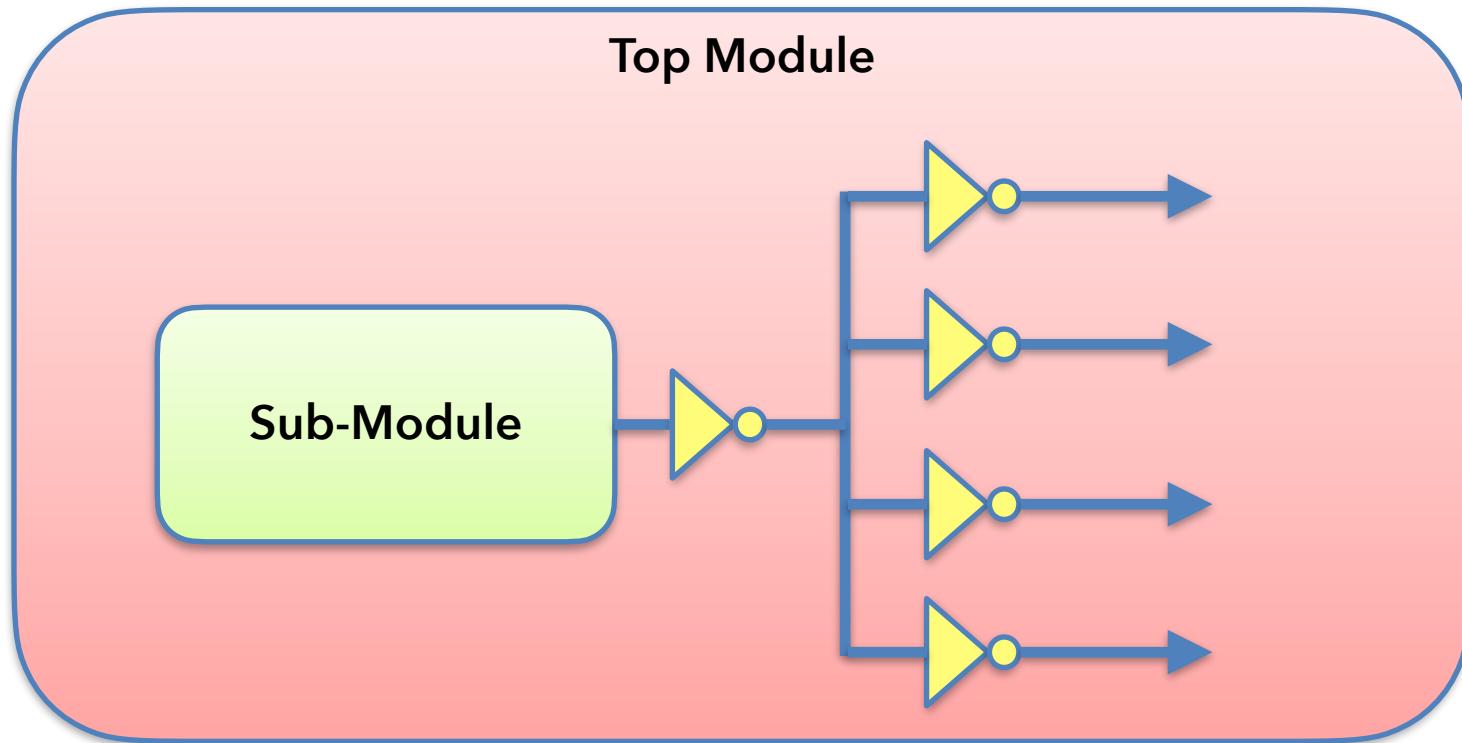- Fan-outs means the number of output wires that a signal drives
- Fan-outs may cause additional delay and power consumption
- The fan-out gates can be **any types of logic gates**



An example of fan-out == 4

Representation of Numbers

- Numbers are represented **UNSIGNED** by default
- Syntax:
 - **<# of bits>'<Radix><Number>**

of bits The number of BINARY bits that the number is comprised of. (default 32 bits)

Radix Radix of the number

b or B:	Binary	E.g., 8'b1011_0011
d or D:	Decimal	E.g., 4'd5
o or O:	Octal	E.g., 3'o5
h or H:	Hexadecimal	E.g., 5'h1A

Number Any legal number in selected (**# of bits**) & (**Radix**)

Agenda

- Gate-Level Design and Basic Concepts
- **Data Flow Modeling**
- Behavioral Modeling
- Sequential Circuits
- Debounce and One-Pulse Circuits
- FPGA Implementation

Today's class will help you:

1. Review the contents of this course

Value Set


- The net types in Verilog can be one of these four states

Net	Reg	Representation
0	0	Logic zero, false condition
1	1	Logic one, true condition
x		Unknown logic value
z		High impedance, floating state

- Please only set the value of a reg to be either **0** or **1**
 - Registers of real circuits do not have values of either **x** or **z**
- It is a better habit to CLEARLY specify the values in Verilog

Net Data Type

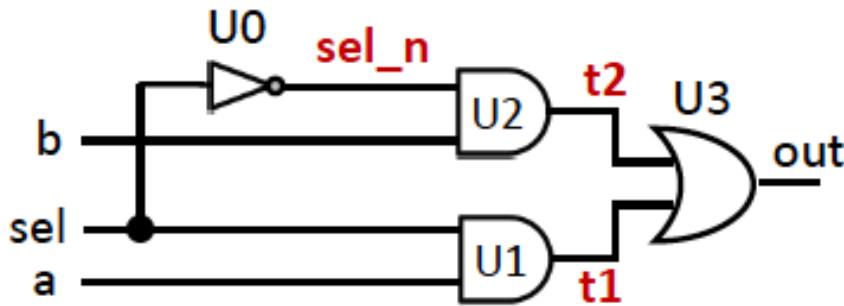- Net type is basically the wires
 - Declare by the keyword **wire** (**CAUTION: NO “wire = 0”**)
- Can be used to connect different modules
- No storage functionality
- Default value is **z**



```
module MUX(out, a, b, sel);
```

```
output out;
```

```
input a,b,sel;
```

```
| wire sel_n,t1,t2;
```

```
not U0(sel_n,sel);
```

```
and U1(t1,a,sel);
```

```
and U2(t2,b,sel_n);
```

```
or U3(out,t1,t2);
```

```
endmodule
```

Register Data Type

- Register data type represents a data storage element **or a net**
 - Depends on how they are used in the **always** block in modules
 - Does not represent anything in a testbench
 - Declare by the keyword **reg** (**CAUTION: NO “reg = 0”**)
- Can have storage functionality
 - If it is a data storage element
- Default value is **x**
- **reg** assignment (=) only occurs in either an **initial** or an **always** block

Register Data Type in Testbench

- Variables of reg data type in testbenches are not synthesized
- They are simply variables to be fed into your modules

```
'timescale 1ns / 1ps
module test_Nand_Latch_1;
reg preset, clear;
wire q, qbar;
Nand_Latch_1 M1 (q, qbar, preset, clear);
always
begin
#20    clear = !clear;
end
initial
begin
#10    preset = 1'b0;  clear = 1'b1;
#10    preset = 1'b1;
end
endmodule
```

// Simulation Unit / Accuracy
// Testbench module
// Inputs should be declared as reg
// Outputs should be declared as wire

// Instantiate YOUR DESIGN module

// always condition: The description always happens
// The value of clear inverts every 20 ns

// Initial conditions

// Units of “Simulation Units”. In this case, 10ns

Vectors

- Both data types can be declared as vectors
 - Similar to what we have done for inputs and outputs
 - Examples
 - `reg [7:0] reg_vector1, reg_vector2;`
 - `wire [5:0] data_bus;`
- You can assign only part of a vector to another

```
wire [7:0] a, b, y;
```


```
assign y[7:4] = a[3:0];
```

```
assign y[3:0] = b[7:4];
```


MSB and LSB

- Vector definition can determine its Most Significant Bit (**MSB**) and Least Significant Bit (**LSB**)
- Important for arithmetic operations

- E.g., `wire [15:0] Bus_A;`

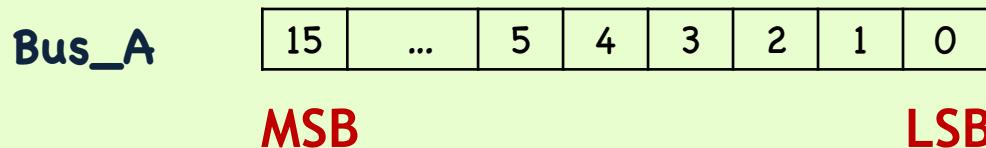

- E.g., `wire [0:15] Bus_B;`

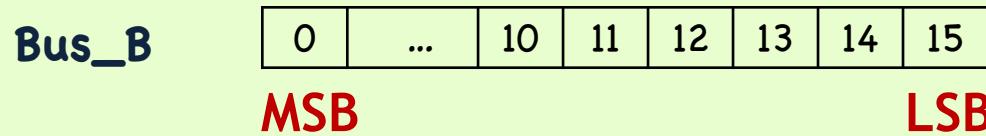

- There is a difference between `Bus_A+1'b1` and `Bus_B+1'b1`

Verilog Modeling

■ Gate level modeling

```
and      a1(OUT, IN1, IN2);  
nand    na1(OUT, IN1, IN2);  
or       or1(OUT, IN1, IN2);
```

■ Data flow modeling

E.g., **assign** a[7:0] = b[7:0] & c[7:0]; (bitwise AND)

■ Behavior modeling (**in always blocks**)

```
E.g.,      if (sel == 1'b1)    begin  
                       S = A;  
                       end  
                       else                 begin  
                       S = B;  
                       end
```

Data Flow Modeling

- For combinational circuits only
- Similar to logic expressions
- Easier for development
- Need to be synthesized to the gate level
- Usage
 - Continuous assignment
 - Conditional assignment
 - Operators

Continuous Assignment

- Syntax:
 - **assign** [the name of **lvalue**] = **rvalue**;
- Assignment can be done for a single wire or a bus
 - **E.g.,** **assign** a[7:0] = b[7:0];
- **lvalue** must be of type **wire** or **output** (but not **reg** type)
- **rvalue** can be an **expression**
 - **E.g.,** **assign** a[7:0] = b[7:0] & c[7:0]; (bitwise AND)
- Cascade is allowed
 - **E.g.,** **assign** {c_out, sum[3:0]} = a[3:0] + b[3:0] + c_in;

Multiple Assignments


- You can do multiple assignments in a single line
 - **assign** S1 = A1 & B1, S2 = A2 | B2, S3 = A3 + B3;
- However, it is a better habit to separate different assignment to different lines

Conditional Operator

- Evaluation depending on the value of condition
 - Syntax:
 - **(Condition) ? (Expression 1) : (Expression 2);**
- TRUE FALSE

```
module simple_mux (F, A, B, Sel);
    input A, B, Sel;
    output F;
    assign F = (Sel == 1'b1) ? A : B;
endmodule
```

Verilog

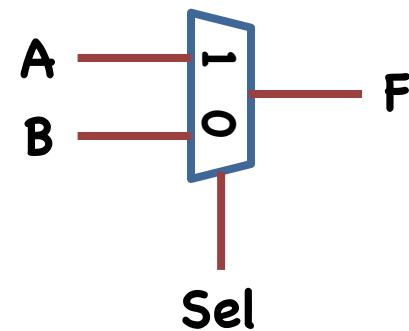

Schematic

Concatenation and Replication

- Assignment can be done by concatenation and replication
 - Concatenation
 - Suppose **A** = 1'b1, **B** = 3'b010
 - assign **Y** = { **A**, 4'hc, **B** }; // **Result Y is 8'b1_1100_010**
 - assign **Y** = { **A**, **B**[0] }; // **Result Y is 2'b10**
 - Replication
 - assign **Y** = { 4{**A**} }; // **Result Y is 4'b1111**
 - assign **Y** = { {2{**A**}}, {2{**B**}}, **A** }; // **Result Y is 9'b1_1_010_010_1**
- * Please note that **Y** should be declared with sufficient bits to accommodate **rvalue**

Agenda


- Gate-Level Design and Basic Concepts
- Data Flow Modeling
- Behavioral Modeling
- Sequential Circuits
- Debounce and One-Pulse Circuits
- FPGA Implementation

Today's class will help you:

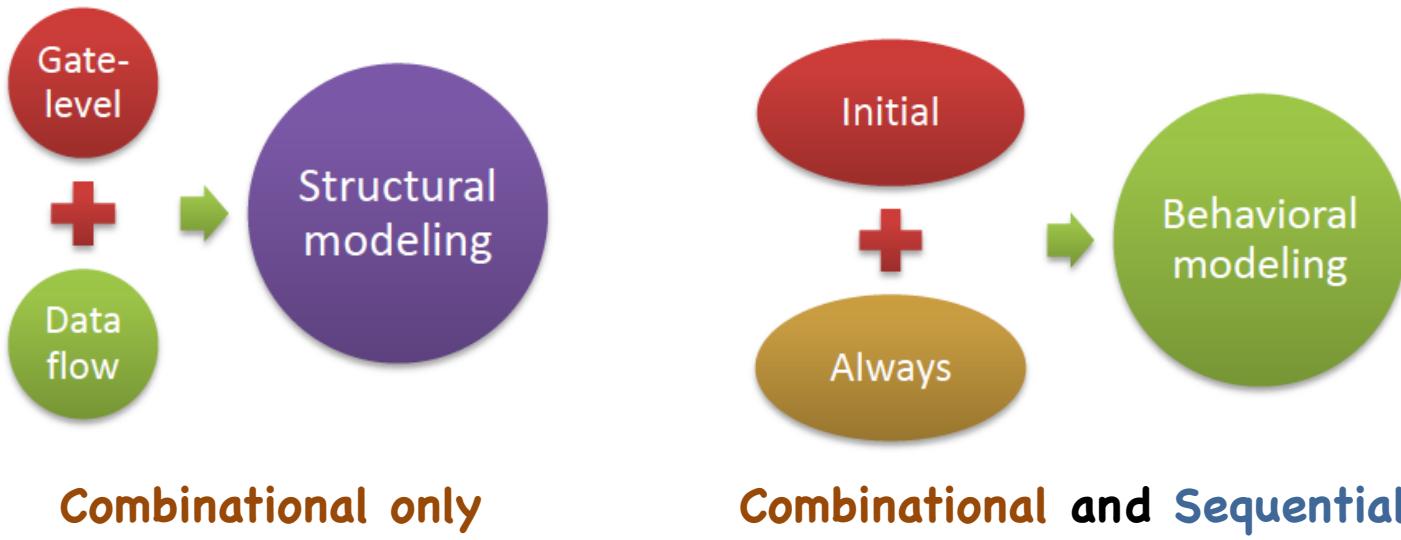1. Review the contents of this course

Behavioral Modeling

- High level description
- Modeling a circuit by its behaviors
- Similar to C++ programming
- Behavioral modeling includes both **combinational** and **sequential** parts



Structural vs. Behavioral Modeling

Structural
modeling

```
{  
    module My_Module(...);  
        ...  
        assign O1 = A+B;          // 1. continuous assignment  
        and   N1(O2, C, D);      // 2. Instantiation of a primitive  
        MUX  M1(O3, Sel, F, G); // 3. Instantiation of a module  
  
    always @ (...)           // 1. always block  
        begin ... end  
  
    initial                 // 2. initial block  
        begin ... end  
  
    endmodule  
}
```


Behavioral
modeling

Behavioral Constructs

- Two constructs: **initial** and **always**
- Similar point:
 - lvalue has to be of **reg** data type
 - Has **begin** and **end**
- **initial**:
 - Used in testbench only
 - Only run once when the testbench begins
- **always**
 - Used both in design and testbench
 - Repeated execution

Register Transfer Level

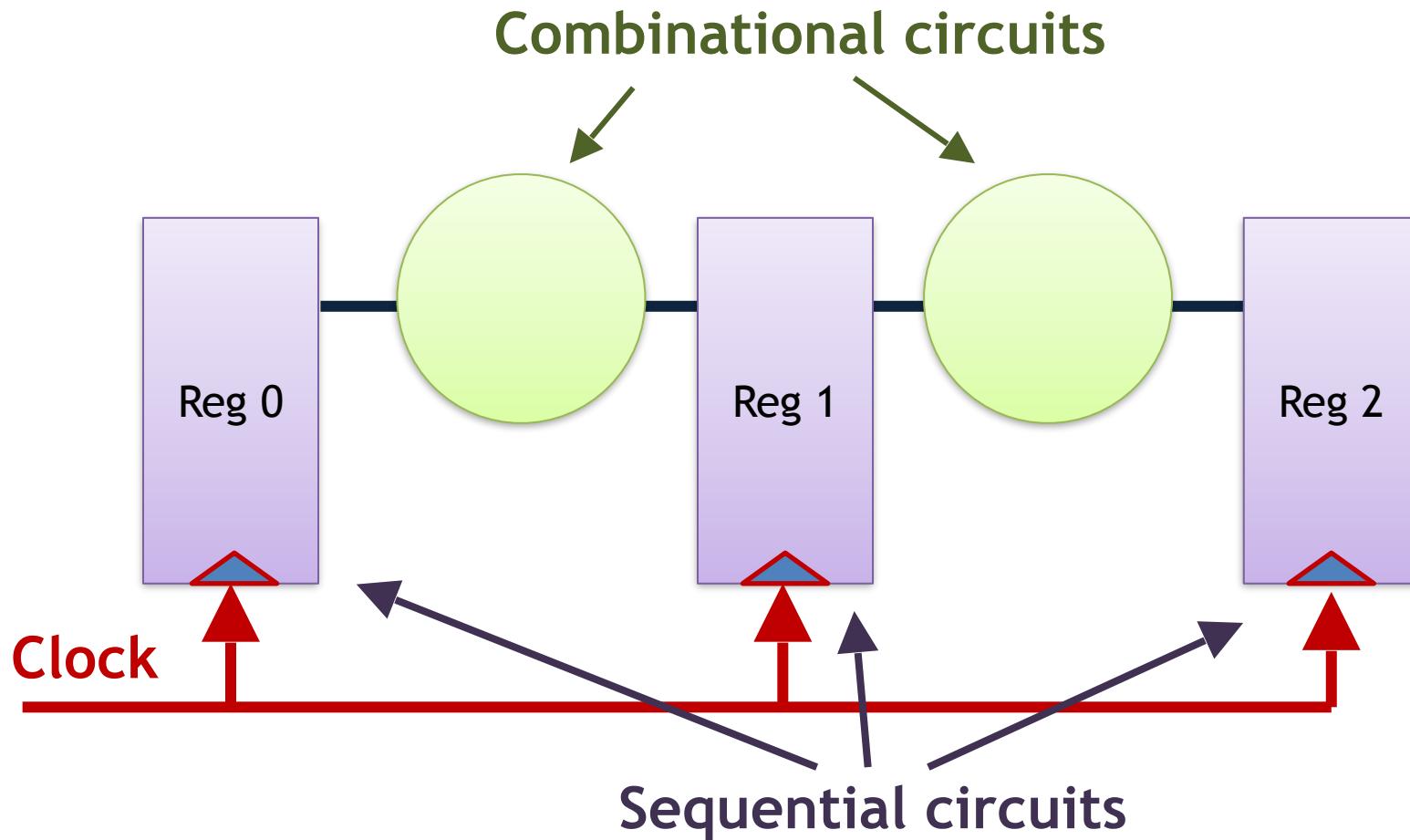- Describes the behavior of combinational circuits between registers



Blocking and Non-blocking

Execute in Order


```
always @ (A or B or C)
begin
```

//Blocking Assignment

```
C = A & B;
```

```
D = !C;
```

```
end
```

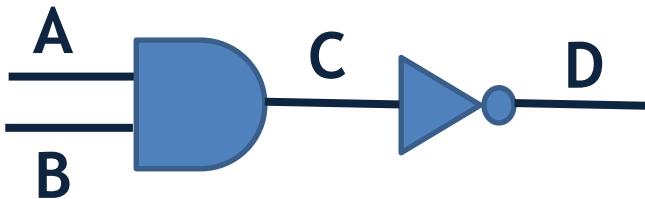

Execute in Parallel


```
always @ (posedge clk)
begin
```

//Non-blocking assignment

```
C <= A & B;
```

```
D <= !C;
```

```
end
```

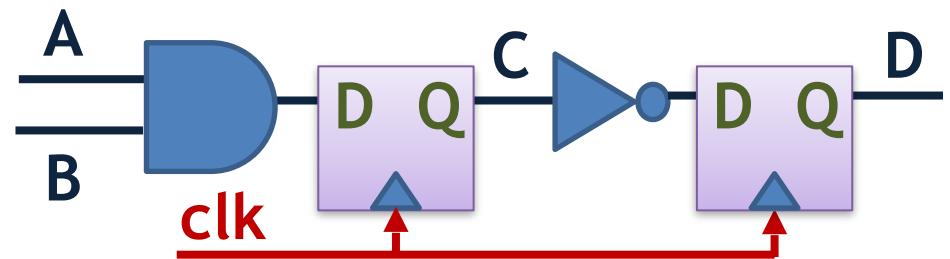

- **NEVER** use blocking and non-blocking assignment in the **SAME** always block

Caution for Always Block

- Combinational circuit: use blocking assignment (**=**) only

```
always @ (A or B or C)
begin
    //Blocking Assignment
    C = A & B;
    D = !C;
end
```

- Sequential circuit: use non-blocking assignment (**<=**) only

```
always @ (posedge clk)
begin
    //Non-blocking assignment
    C <= A & B;
    D <= !C;
end
```

Sensitivity List

- Wakes up an always block and do the execution
- **For combinational circuit only**
- Separated by **or**
- Variables include:
 - Right hand side of “=”
 - Condition variables in **if**
 - Condition variables in **case**

```
always @ (A or B or C or Sel or Sel_Bus)
begin
    C = A & B;
    if (Sel) begin
        D = !C;
    end
    case (Sel_Bus)
        .....
    endcase
end
```

- No need of sensitivity list for **always @(*)**

Procedural Statements

- Control operators similar to C++
- Not all of the operators can be used in your design
- Any operator used in the design must be **synthesizable**
 - However, you can use non-synthesizable operators in testbenches

Operator	Design	Testbench	Synthesized to
If-else	Yes	Yes	Mux
case	Yes	Yes	Mux or Decoder
for	No	Yes	N/A
while	No	Yes	N/A
repeat	No	Yes	N/A


If-Else Statement

```
if (condition1)
begin
<expression> ;
end
else if (condition2)
begin
<expression> ;
end
else
begin
<expression> ;
end
```

```
module MUX3(out, a, b, sel);
output    out;
input     a,b,sel;
reg      out;

always @(*) begin
if(sel == 1'b1)
    out = a;
else
    out = b;
end


endmodule
```

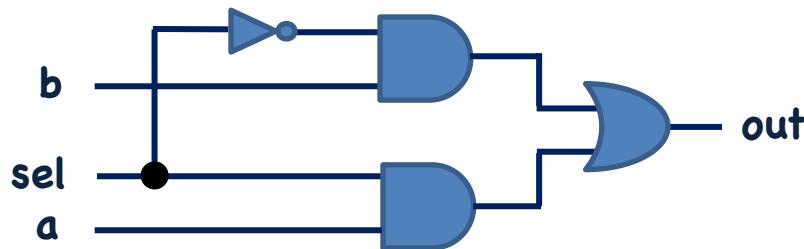

Synthesized to a **MUX**

Case Statement
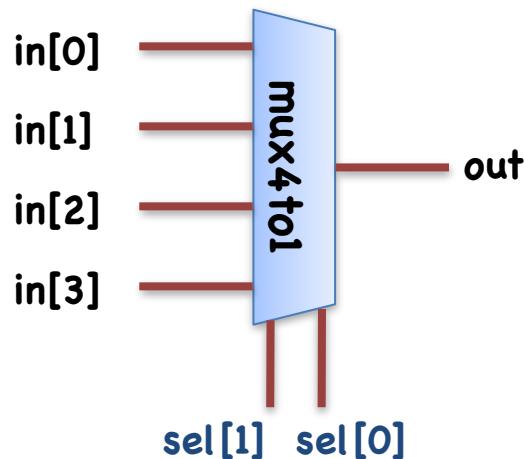
```
case (condition)
    alternative1: <expression> ;
    alternative2: <expression> ;
    ...
    default: <expression> ;
endcase
```



Synthesized to a MUX

```
module mux4to1 (out, in, sel);
    output      out;
    input [3:0]  in;
    input [1:0]  sel;
    reg         out;

    always @(*) begin
        case (sel)
            2'd0 :          out = in[0];
            2'd1 :          out = in[1];
            2'd2 :          out = in[2];
            default :       out = in[3];
        endcase
    end

endmodule
```

Case Statement (Cont'd)



Din[1:0]	Dout[3:0]
00	0001
01	0010
10	0100
11	1000

Synthesized to a **DECODER**


```
module mux4to1 (Dout, Din);  
  
output [3:0] Dout;  
input [1:0] Din;  
reg [3:0] Dout;  
  
always @(*) begin  
    case (Din)  
        2'd0 : Dout = 4'b0001;  
        2'd1 : Dout = 4'b0010;  
        2'd2 : Dout = 4'b0100;  
        default : Dout = 4'b1000;  
    endcase  
end  
  
endmodule
```

Unintended Latch

- Clearly specify every situations in **if-else** or **case** statements
- Incomplete statements lead to **unintended latch**

```
always @ (sel_a or sel_b or  
          data_a or data_b)  
  
begin  
  
    case ({sel_a, sel_b})  
        2'b10: y_out = data_a;  
        2'b01: y_out = data_b;  
    endcase  
  
end
```

Synthesis result:

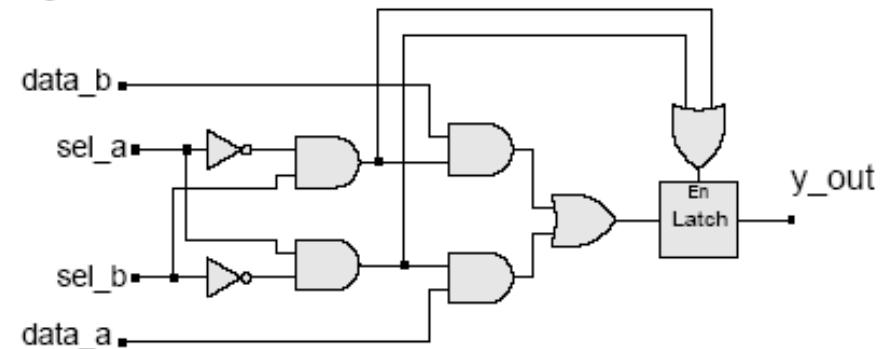

Loop Statements

- Not synthesizable
- Used in testbench only

For loop

```
reg [15:0] x;  
integer i;  
  
initial  
begin  
    x = 16'd0;  
    for ( i = 0; i <=10; i = i + 1 )  
        begin  
            x = x + 1'b1;  
        end  
    end
```

Repeat loop

```
reg [15:0] x;  
  
initial  
begin  
    x = 16'd0;  
    repeat ( 16 )  
        begin  
            #2  
            x = x + 1'b1;  
        end  
    end
```

While loop

```
reg [15:0] x;  
  
initial  
begin  
    x = 16'd0;  
    while ( x <= 20 )  
        begin  
            #2  
            x = x + 1'b1;  
        end  
    end
```

Constants

- Declare with keyword parameter
- Similar to **const** in C++
 - On the other hand, **`define** is similar to **#define** in C++
- Value does not change during simulation
- Can be used in vector declaration
 - Easier in project development and maintenance

```
parameter size = 16;  
reg [size-1:0] a; // vector declaration  
parameter b = 2'b01;  
parameter av_delay = (min_delay + max_delay) / 2;
```

Delay Control Operator

- # followed by units of time
- Specify the delay in terms of units specified by `timescale
- NOT synthesizable, only used in testbench
- In real circuits, delay is realized by buffers (two inverters)

```
...
always
  begin
    #0   clock = 0;
    #50  clock = 1;
    #50;
  end
...
...
```

```
...
always
  begin
    #clock_period/2;
    clock = ~clock;
  end
...
...
```

parameter
clock_period



Caution of Assignments



// Error version

module FullAdder(*s*, *co*, *a*, *b*, *ci*);

input *a*, *b*, *ci*;

output *s*, *co*; **Error continuous assignment!**

s = *a* ^ *b* ^ *ci*;



always @(*a* or *b* or *ci*) begin

assign *co* = (*a&b*)|(*b&ci*)|(*a&ci*);

end

Error procedural assignment!

endmodule

// Correct version

module FullAdder(*s*, *co*, *a*, *b*, *ci*);

input *a*, *b*, *ci*;

output *s*, *co*;

reg *co*; **lvalue of procedural assignment must be reg**

assign *s* = *a* ^ *b* ^ *ci*;

always @(*) begin

co = (*a&b*)|(*b&ci*)|(*a&ci*);

end

endmodule

Combinational Circuits (1/2)

- You have **three ways** to model a combinational circuit
 - You will be good if you remember them

1. Gate-level modeling

- `not N1(out, in);`
- `nand N2(out, in1, in2);`
- `or N3(out, in1, in2, in3);`
- etc.

2. Continuous assignment

- Declare your **lvalues** as **wire** data type
- **assign lvalue = (your logic expression);**

Combinational Circuits (2/2)

3. Use always block

- Declare your **lvalues** as **reg** data type
- Only use "**=**" in your assignment expressions
- Avoid using "**<=**" in your expressions

Correct

```
reg lvalue;  
  
always @ (*)  
begin  
    lvalue = (your expression);  
end
```



Wrong

```
wire lvalue;  
  
always @ (*)  
begin  
    assign lvalue <= (your expression);  
end
```



1. lvalue should be **reg**
2. Can't use **assign**
3. Avoid "**<=**"

Agenda

- Gate-Level Design and Basic Concepts
- Data Flow Modeling
- Behavioral Modeling
- **Sequential Circuits**
- Debounce and One-Pulse Circuits
- FPGA Implementation

Today's class will help you:


1. Review the contents of this course

What is Sequential Circuit?

	Sequential	Combinational
Clock	Yes	No
Memory elements	Yes	No
Always block assignment	Non-blocking \ll	Blocking $=$
Continuous assignment	Not available	<code>assign lvalue = rvalue</code>

- Memory element
 - Stores "1" or "0"
 - Latch and Flip-Flop
 - Usually triggered by clock signals

Basic Sequential Circuit

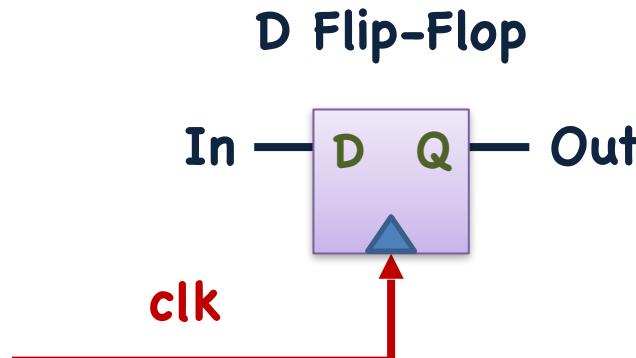


```
always @ (posedge clk)
```

```
begin
```

//Non-blocking assignment


```
Out <= In;
```

```
end
```

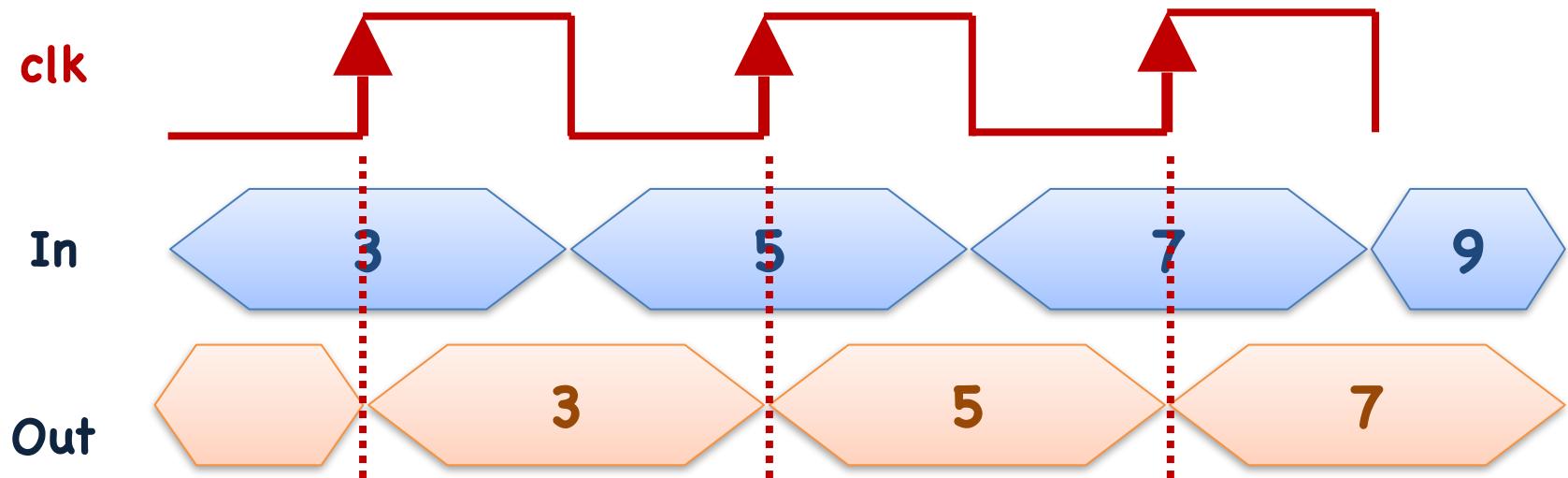


Latch and D Flip-Flop

- Latch: triggered by **level**

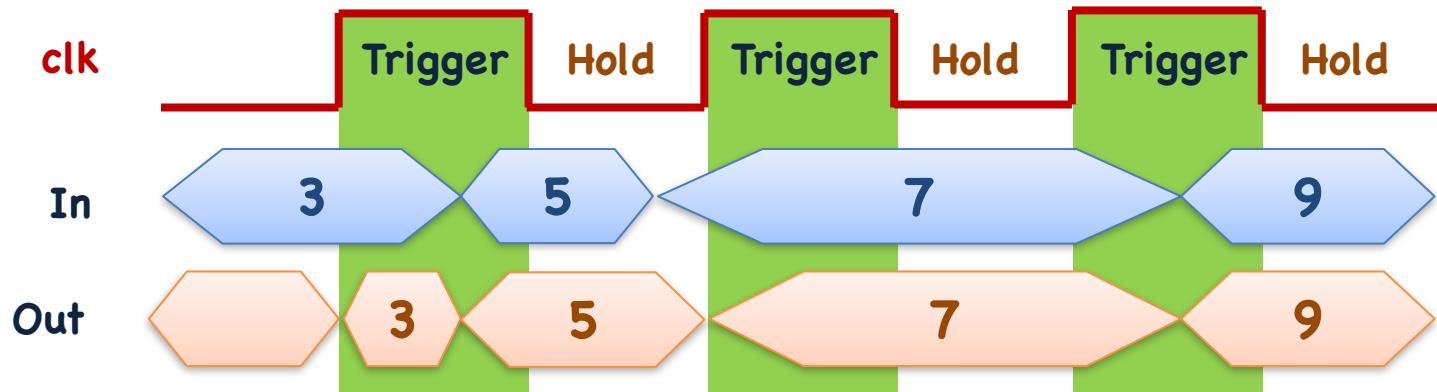

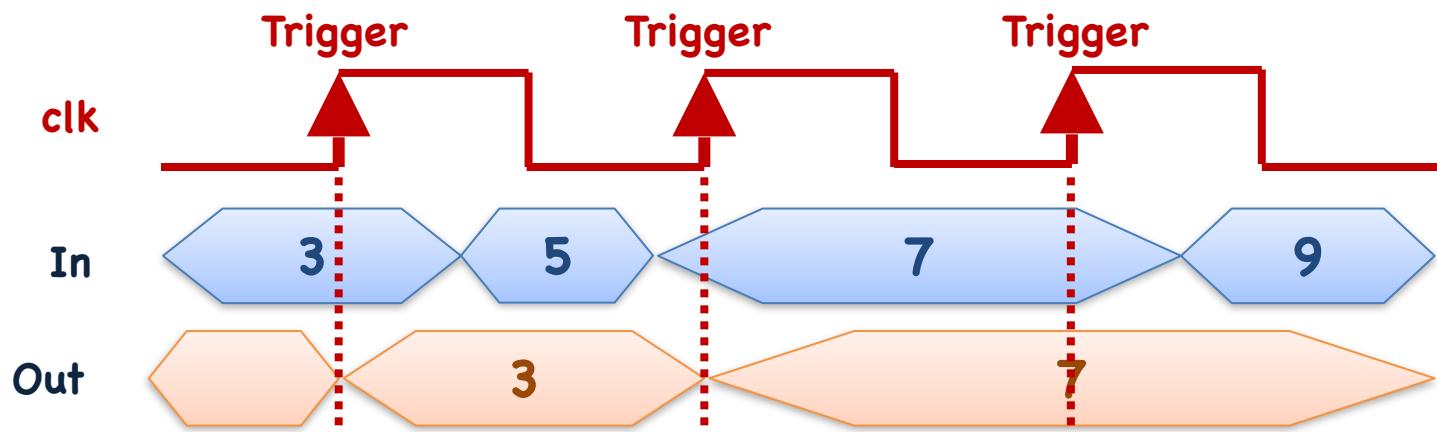- D Flip-Flop: triggered by **clock edge**



D Flip Flop

- Changes its value at the clock edges

Positive-edge triggered D Flip-Flop
Truth table


Clk	D	Q(t+1)
↑	0	0
↑	1	1
0	-	Q(t)
1	-	Q(t)

Negative-edge triggered D Flip-Flop
Truth table


Clk	D	Q(t+1)
↓	0	0
↓	1	1
0	-	Q(t)
1	-	Q(t)

Edge-Trigger in Always Block

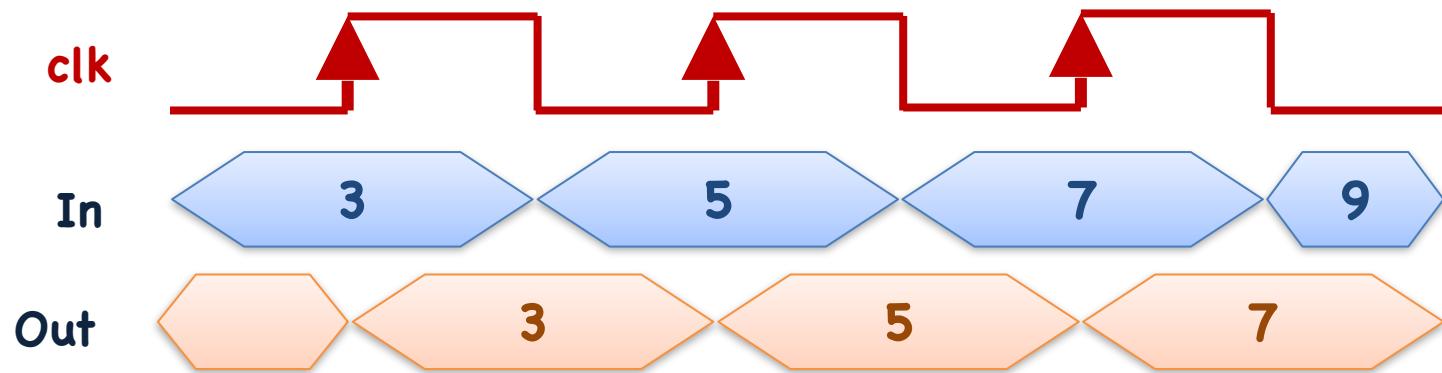- Positive-edge trigger: use **posedge** in your always block




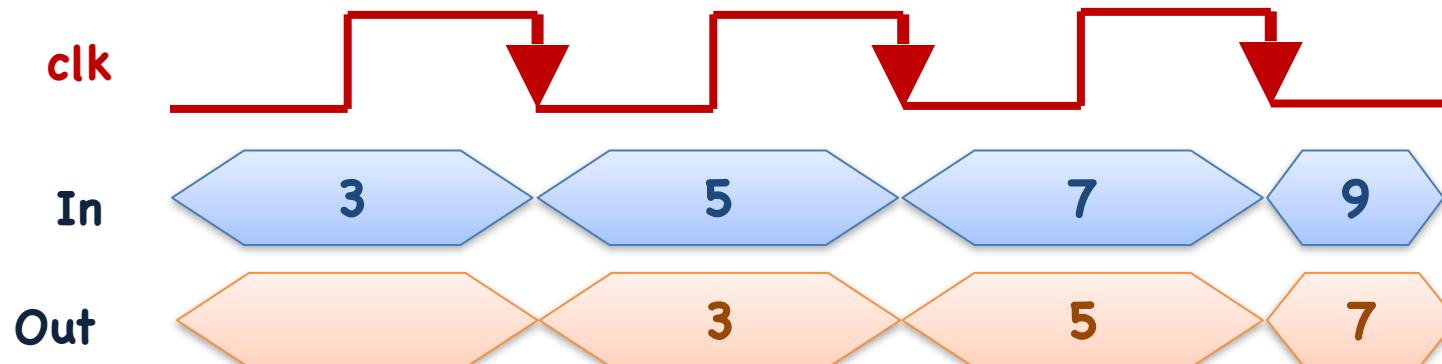- Negative-edge trigger: use **negedge** in your always block




Latches in a D Flip-Flop

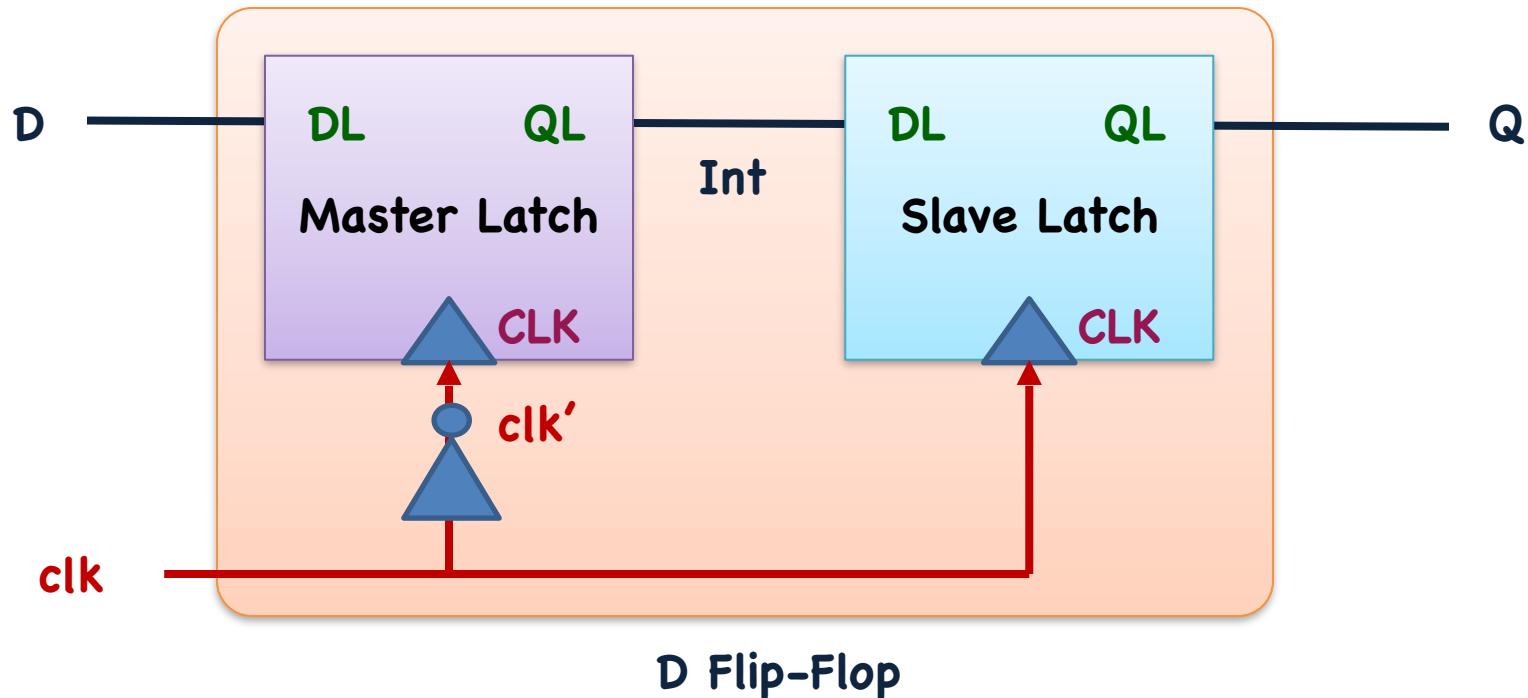- A positive-edge triggered D Flip-Flop consists of two latches
 - The master latch is triggered by clk'
 - The slave latch is triggered by clk
- Two level triggered latches form an edge-triggered Flip-Flop




Flip-Flop Timing Diagram

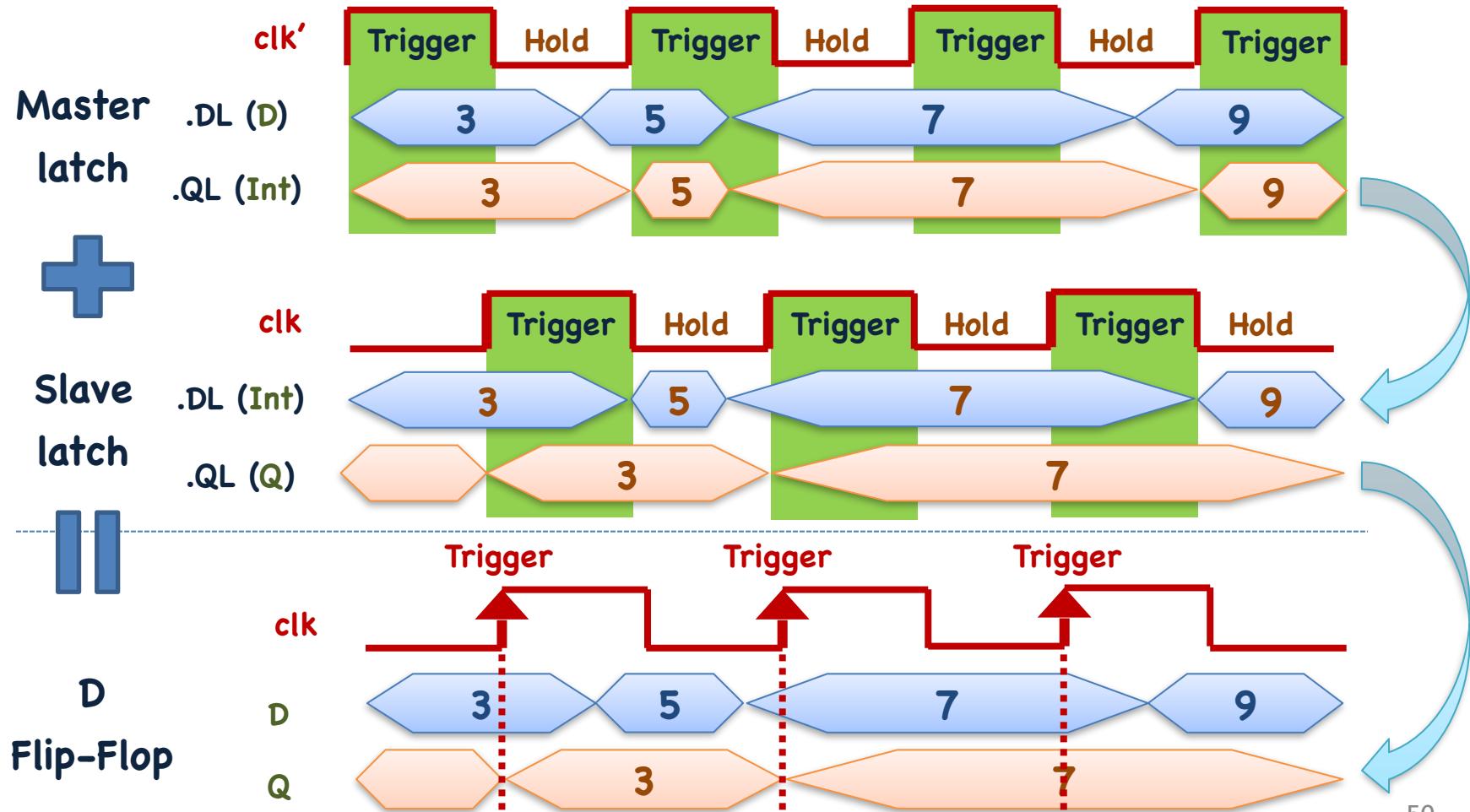- A timing diagram from the master latch to slave latch



Register Transfer Level

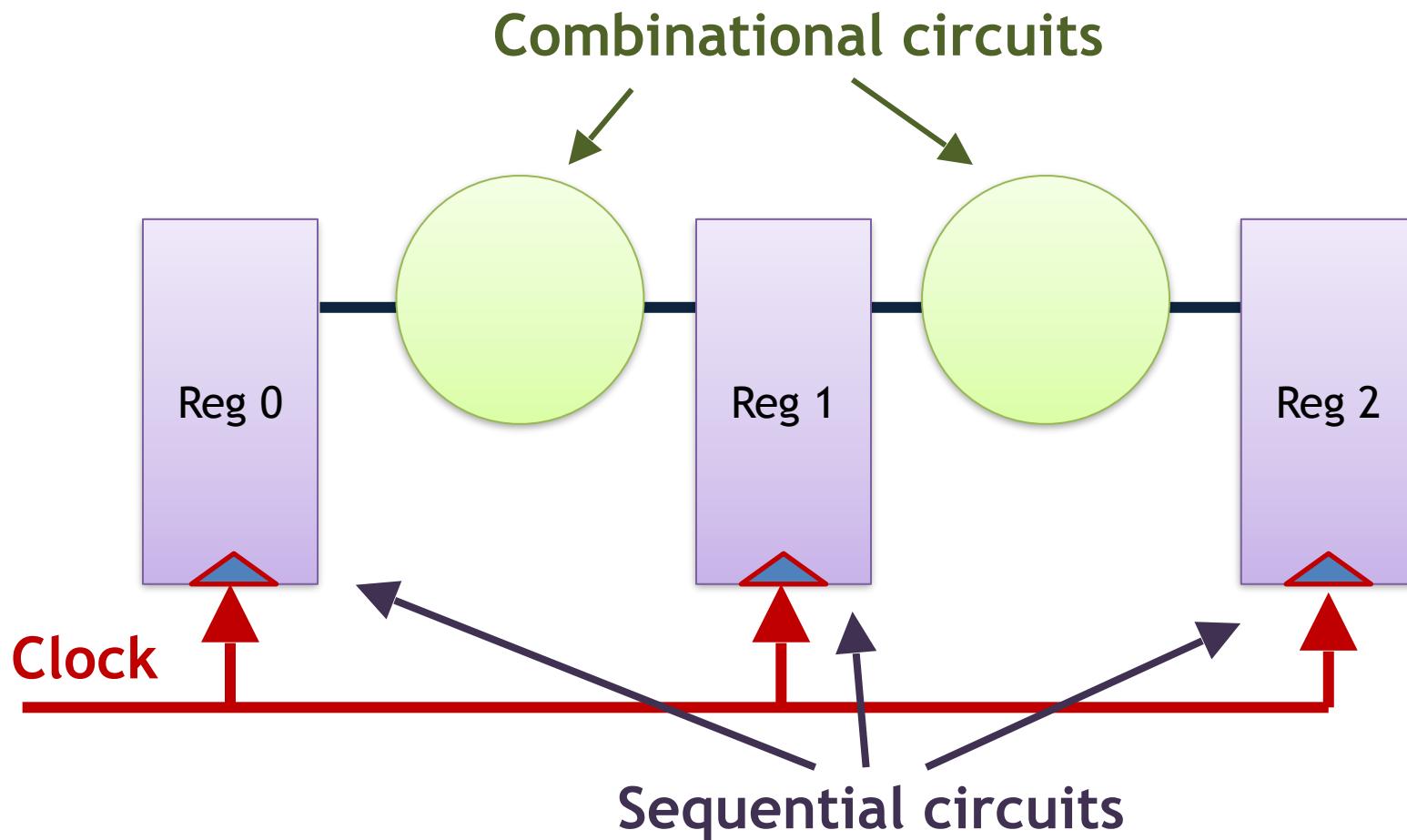- Describes the behavior of combinational circuits between registers



Blocking and Non-blocking

Execute in Order


```
always @ (A or B or C)
begin
```

//Blocking assignment

```
C = A & B;
```

```
D = !C;
```

```
end
```

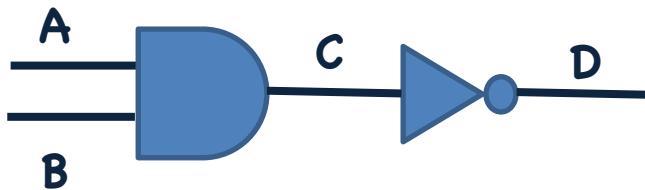

Execute in Parallel


```
always @ (posedge clk)
begin
```

//Non-blocking assignment

```
C <= A & B;
```

```
D <= !C;
```

```
end
```

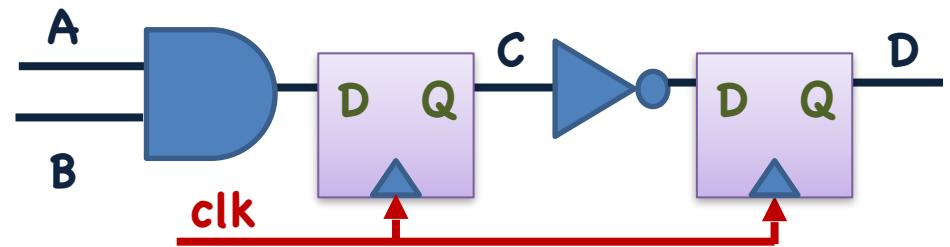

- **NEVER** use blocking and non-blocking assignment in the **SAME** always block



Bad and Good Examples



```
// blocking assignment  
always @(posedge clk) begin  
    M = A & B;  
    Y = M | C;  
end
```



```
// non-blocking assignment  
always @(posedge clk) begin  
    M <= A & B;  
    Y <= M | C;  
end
```

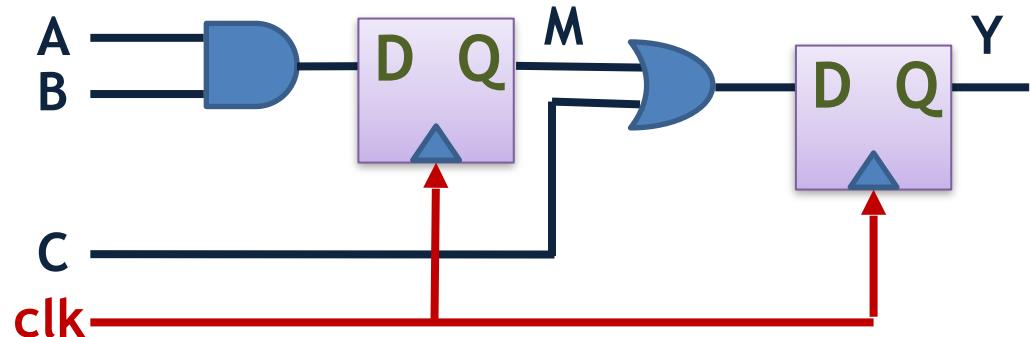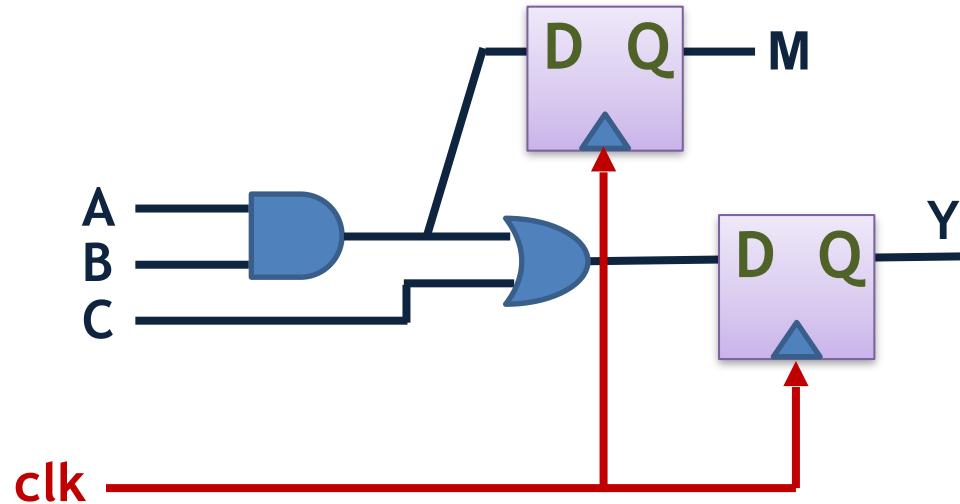


Initialize Flip-Flops

- For combinational circuits, we initialize the inputs of modules by initial blocks in the testbench
- For sequential circuits, a **reset signal** is necessary
 - Initialize the reset signal (i.e. your module) first in your testbench
- Two reset methods
 - Synchronous reset
 - Asynchronous reset


Synchronous Reset

- Reset the value stored in a D Flip-Flop to 0
- Triggered by clock edges
- Assume that **Q = 1'b0** when Reset is set to 1'b0

Scheme 1

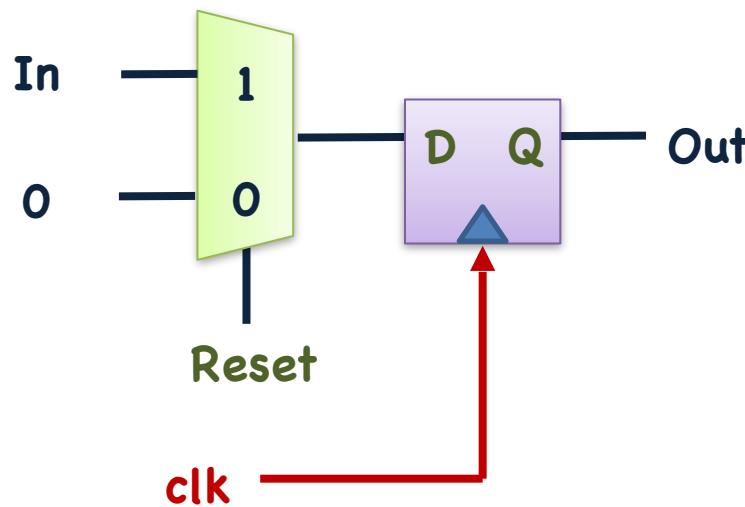

Scheme 2

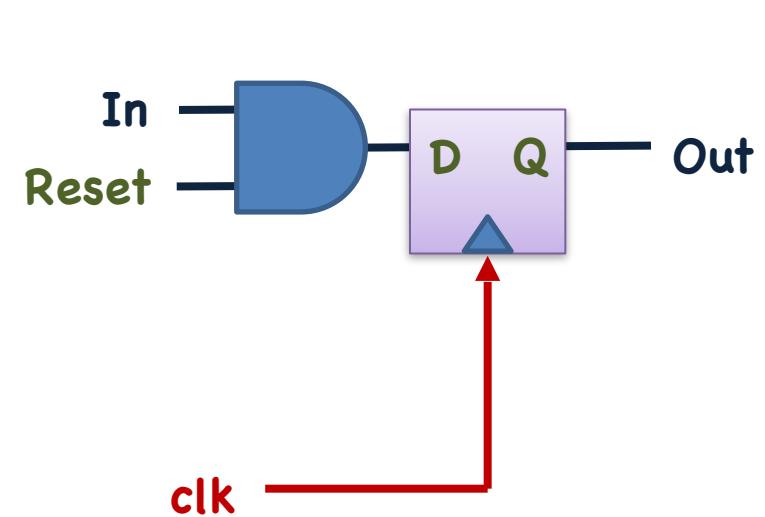


Synchronous Reset in Always Block

- Prioritize your reset signal over the rest of the inputs
- In your testbench, initialize your reset signal first
- You shall not use any initial block in your design modules


```
module My_Test_Flip_Flop (Out, In, clk, Reset);
    input    In, clk, Reset;
    output   Out;
    reg      Out;

    always @ (posedge clk)      ← Behavior
        begin
            if (Reset == 1'b0)          Out <= 1'b0;
            else                         Out <= In;
        end
    endmodule
```


Declaration of
Synchronous

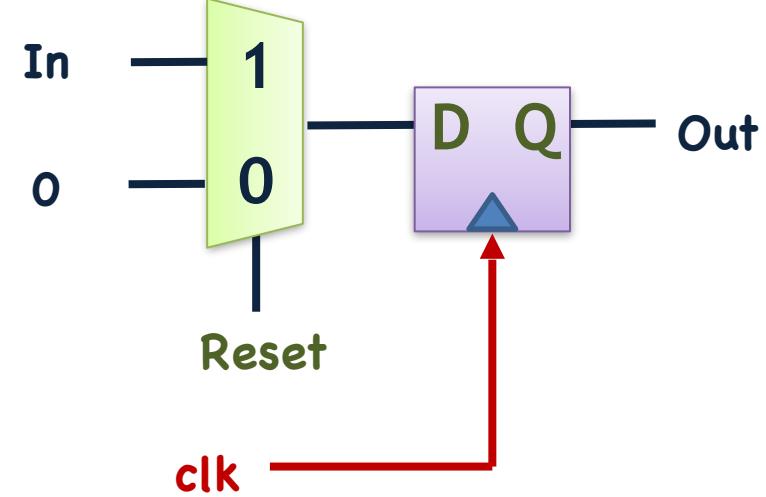

Synchronous vs. Asynchronous Reset

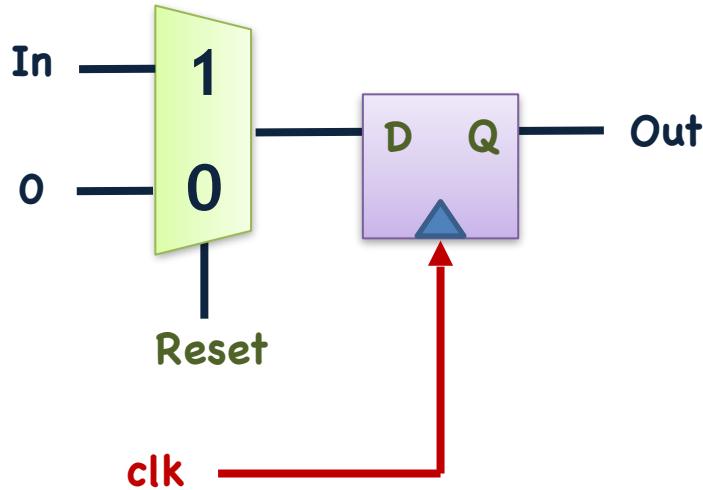

Synchronous Reset

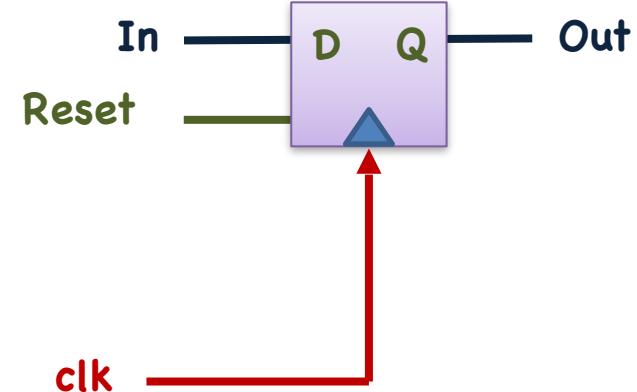

Asynchronous Reset

	Synchronous Reset	Asynchronous Reset
Clock	Reset at clock edges	Regardless of clock
Always block	always @ (posedge clk)	always @ (posedge clk or posedge Reset)
Logic	Additional Mux or AND gate	Additional reset input port in DFF


Example: 3-Bit Counter

```
module Counter_3Bit(clk, Reset, num);
input      clk, Reset;
output     [2:0] num;
reg       [2:0] num;
wire      [2:0] next_num;

always @ (posedge clk) begin
    if (!Reset)
        num <= 1'b0;
    else
        num <= next_num;
end

assign   next_num = num + 1'b1;

endmodule
```

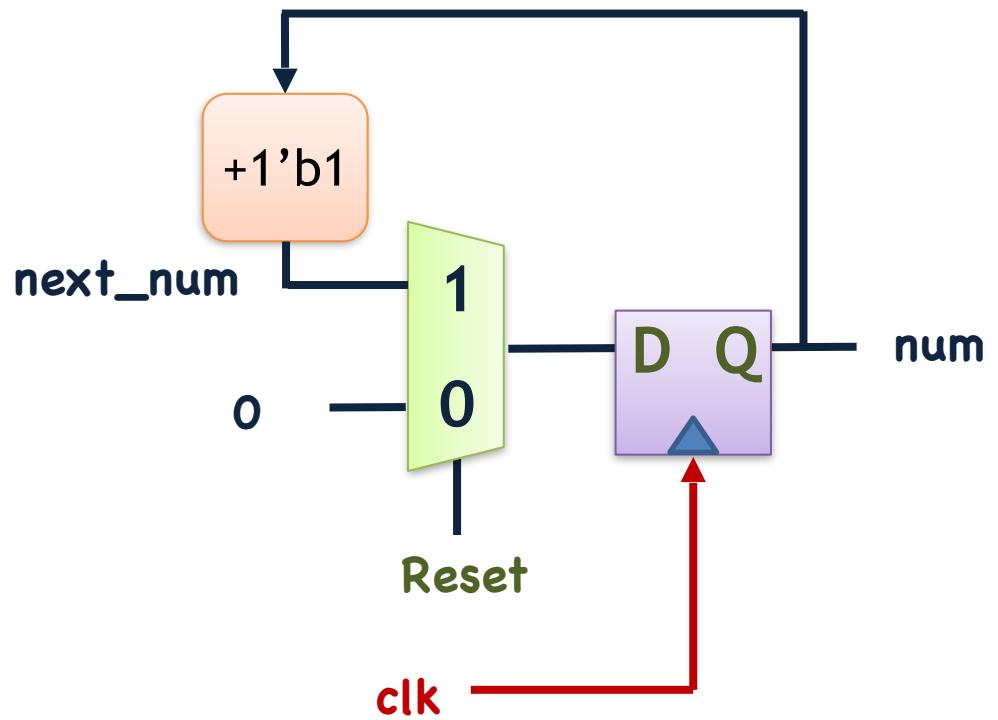

Agenda


- Gate-Level Design and Basic Concepts
- Data Flow Modeling
- Behavioral Modeling
- Sequential Circuits
- Debounce and One-Pulse Circuits
- FPGA Implementation

Today's class will help you:

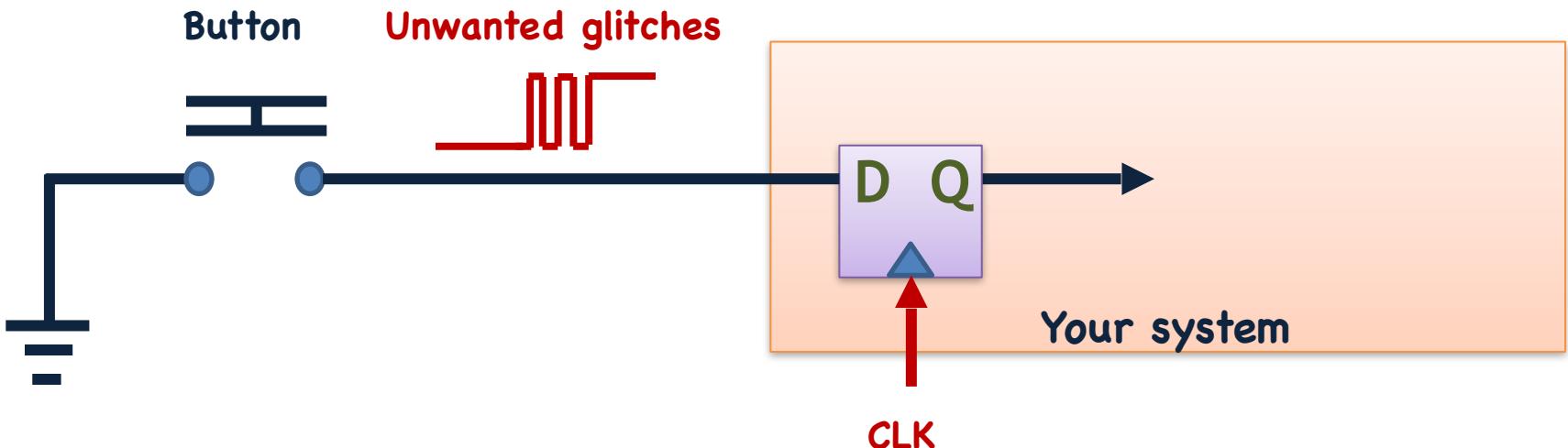1. Review the contents of this course


Push Buttons

- Several push buttons are available as inputs on FPGA
- Map push buttons to your inputs using .xdc file
- Need to handle **meta-stability (glitches)** problem



Handling Meta-Stability

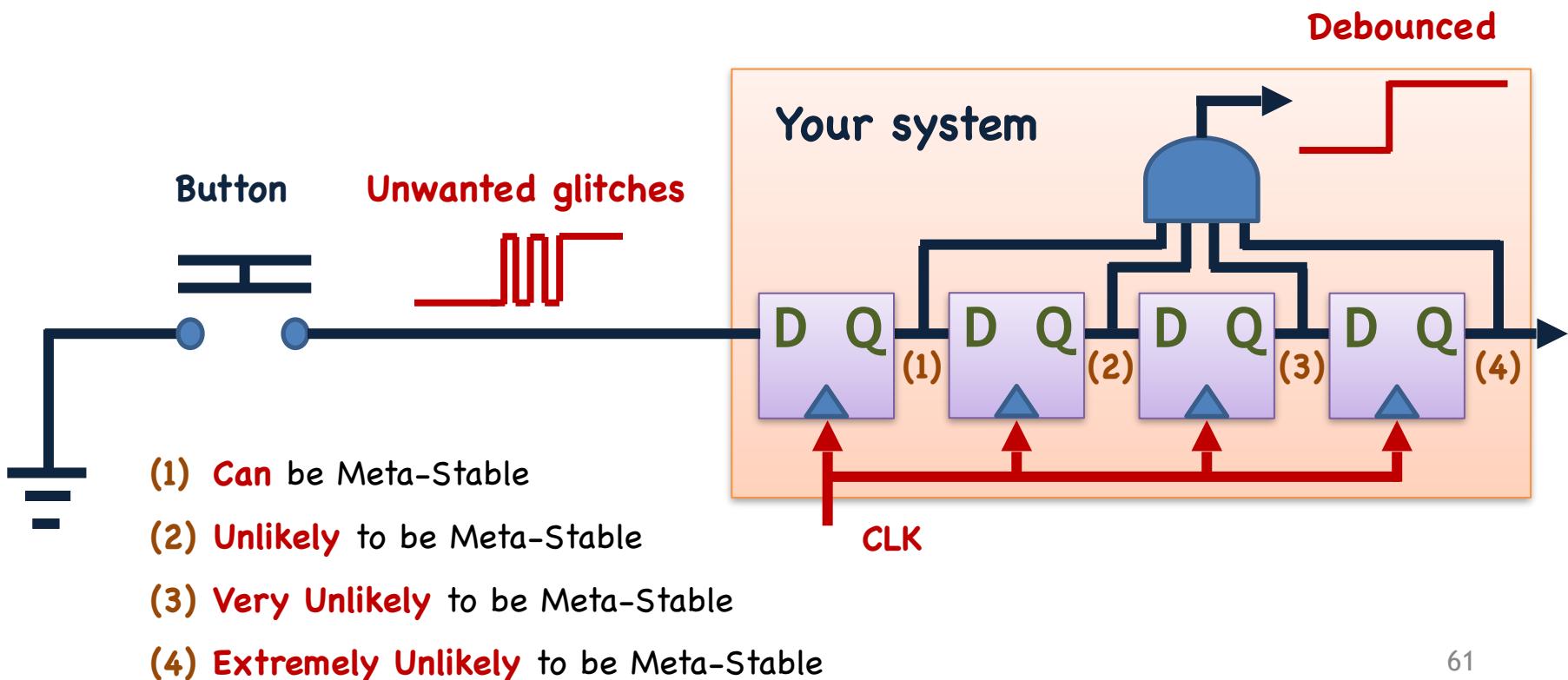- Debounce circuit
- Shift registers to allow time for signals to stabilize
- Detect if DFF chains are all ones or zeros



Verilog Code for Debounce Circuit

```
module debounce (pb_debounced, pb, clk);

    output  pb_debounced;          // signal of a pushbutton after being debounced
    input   pb;                  // signal from a pushbutton
    input   clk;

    reg [3:0] DFF;              // use shift_reg to filter pushbutton bounce


    always @(posedge clk)
        begin
            DFF[3:1] <= DFF[2:0];
            DFF[0]   <= pb;
        end

    assign pb_debounced = &DFF;



endmodule
```

One Pulse Circuit

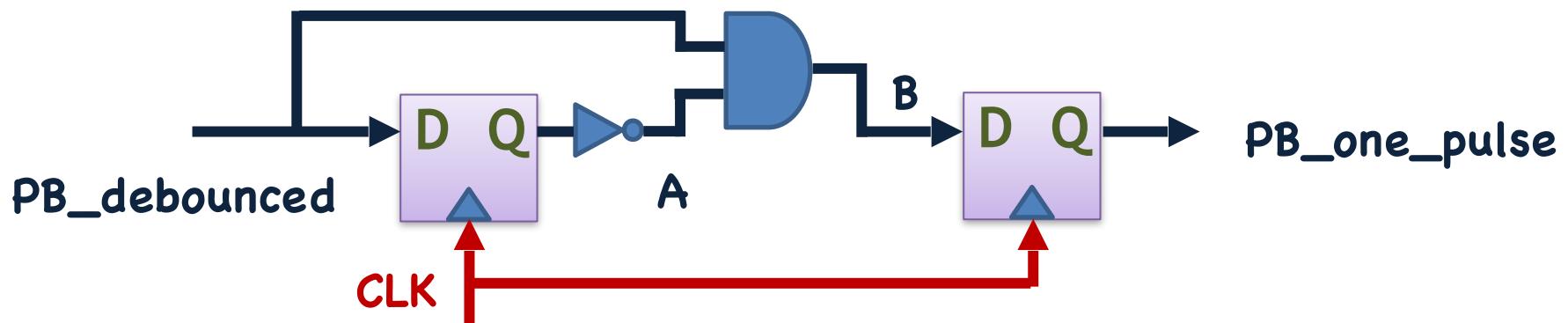- The one pulse circuit generates a one-clock-cycle pulse when the push button is pressed
 - A push button is usually pressed for many clock cycles
- The circuit is used when we want to trigger only once



One Pulse Circuit (Cont'd)

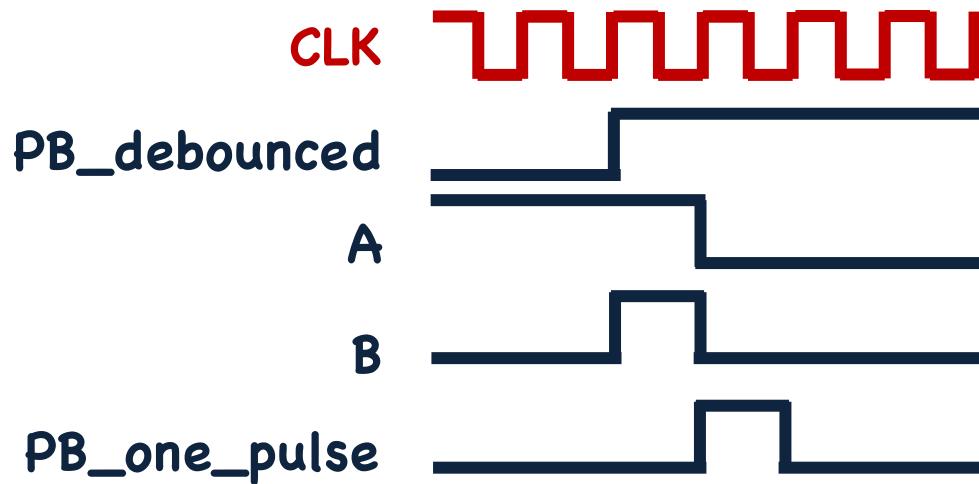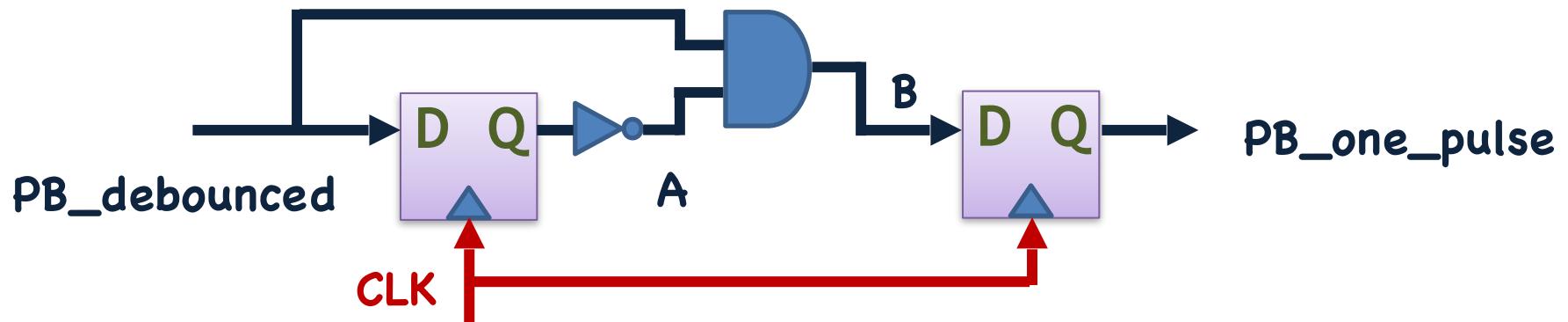

Verilog Code

```
// One-pulse circuit
module onepulse (PB_debounced, CLK, PB_one_pulse);
    input          PB_debounced;
    input          CLK;
    output         PB_one_pulse;
    reg           PB_one_pulse;
    reg           PB_debounced_delay;

    always @ (posedge CLK) begin
        PB_one_pulse <= PB_debounced & (! PB_debounced_delay);

        PB_debounced_delay <= PB_debounced;
    end
endmodule
```

Agenda


- Gate-Level Design and Basic Concepts
- Data Flow Modeling
- Behavioral Modeling
- Sequential Circuits
- Debounce and One-Pulse Circuits
- **FPGA Implementation**

Today's class will help you:

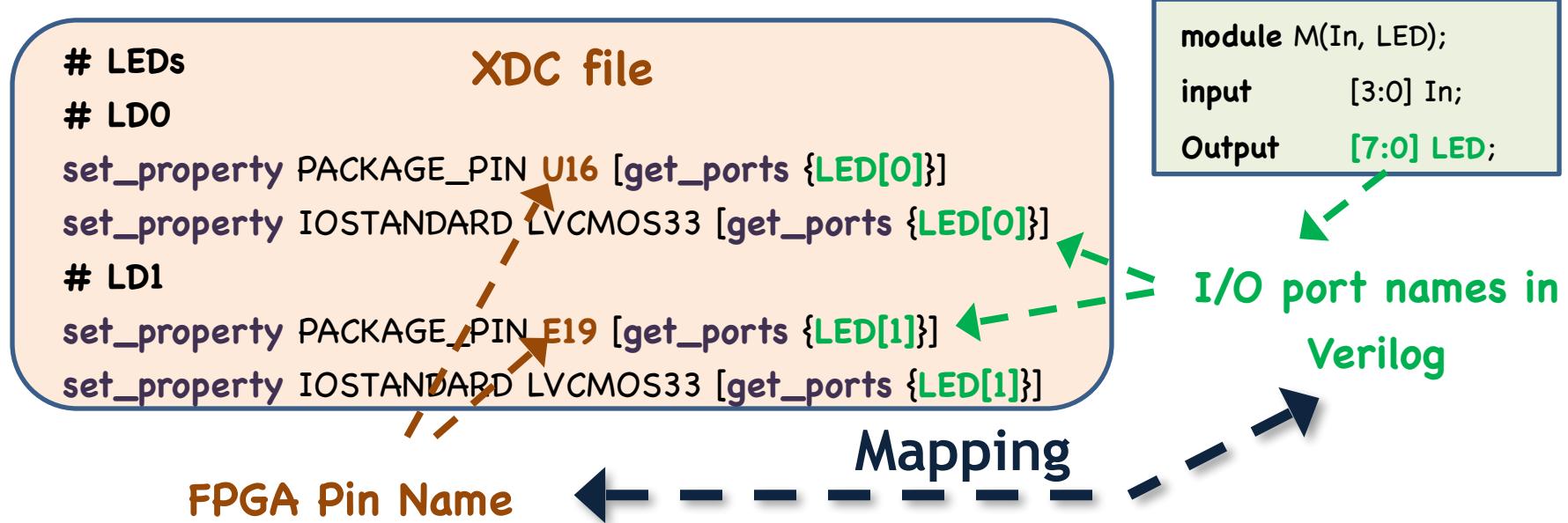1. Review the contents of this course

Port Mapping


- Maps your inputs and outputs to FPGA pins
 - One-to-one mapping
- Defined in an **XDC** (Xilinx Design Constraints) file



7-Segment Display Control (1/2)

- Four enable signals for the four display units
 - AN[3:0] correspond to **the four digits**
 - AN is used to **ENABLE** one of the four digits
 - Set one bit of AN[3:0] to **LOW** to illuminate one digit


AN Bit	FPGA Pin
3	W4
2	V4
1	U4
0	U2

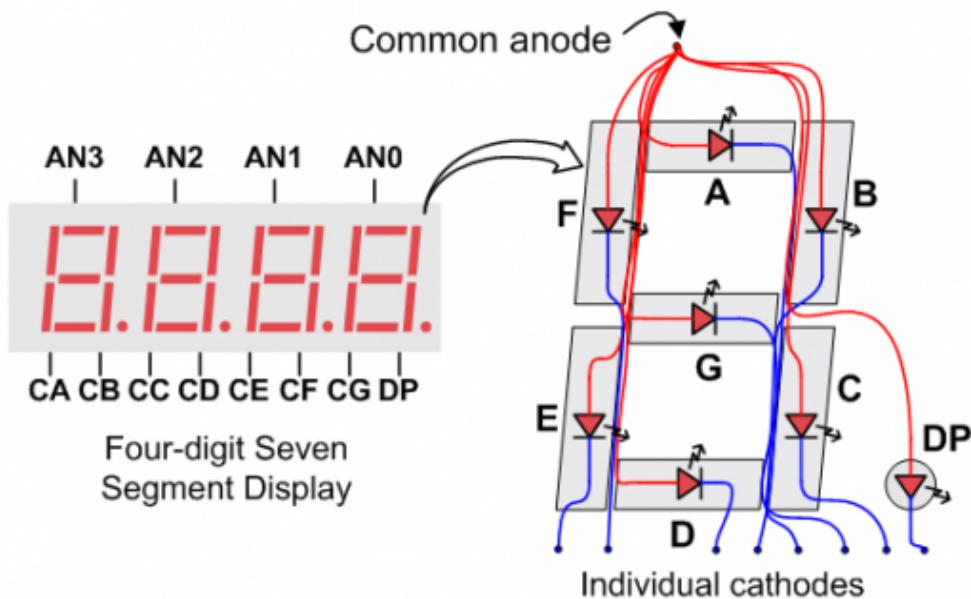

Digit	AN[3:0]
3	0111
2	1011
1	1101
0	1110

7-Segment Display Control (2/2)

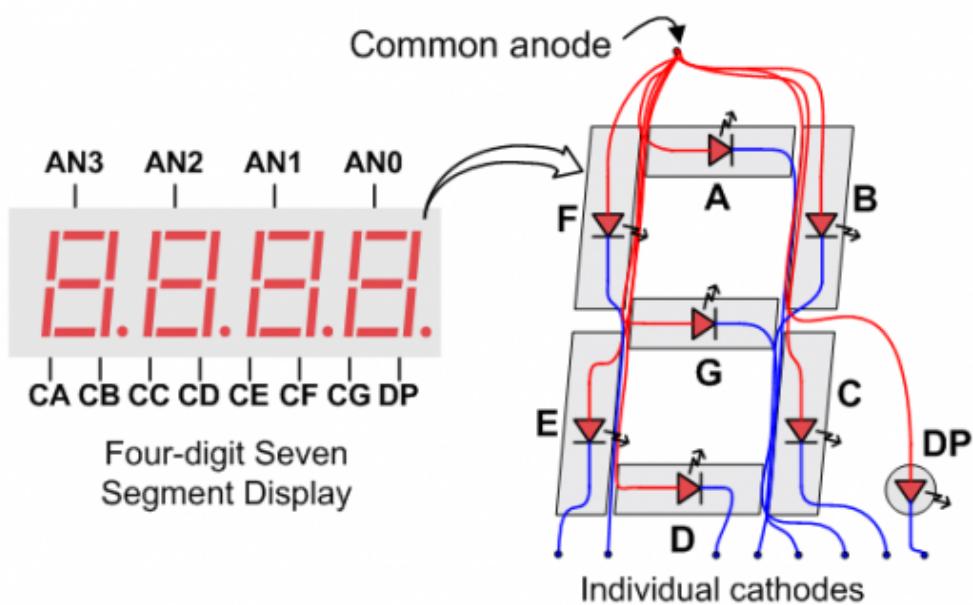
- Eight signals for the segments and dot
 - **seg[0:6]** in the XDC file correspond to **segments A~G** shown below
 - **dp** in the XDC file corresponding to **DP (dot)**
 - To illuminate a segment, set its value to **LOW**



Symbol	FPGA Pin
CA	W7
CB	W6
CC	U8
CD	V8
CE	U5
CF	V5
CG	U7
DP	V7

Display Four Digits Concurrently

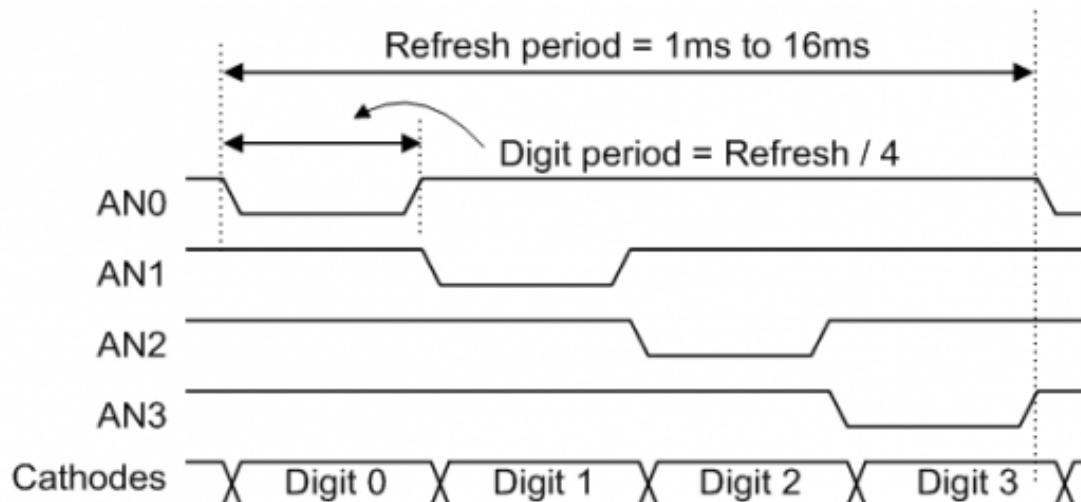- Time multiplexing
- Use a **mux** and **clock divider**
 - **Mux** to select the digit to display (i.e. set which **AN** bit to low)
 - **Clock divider** to display at the right refresh frequency (**1ms to 16ms**)
- The clock provided by Basys 3 is **100MHz**
 - That is, **10ns** per clock cycle
 - Generate a clock with a frequency of **$1/2^{17}$ clk**



*Pictures cited from www.xilinx.com for education purpose only

Thank you for your attention!



*Taken at Yosemite Valley Village at Yosemite, California, USA.
This picture is taken by Chun-Yi Lee himself, who is also a fan of photography